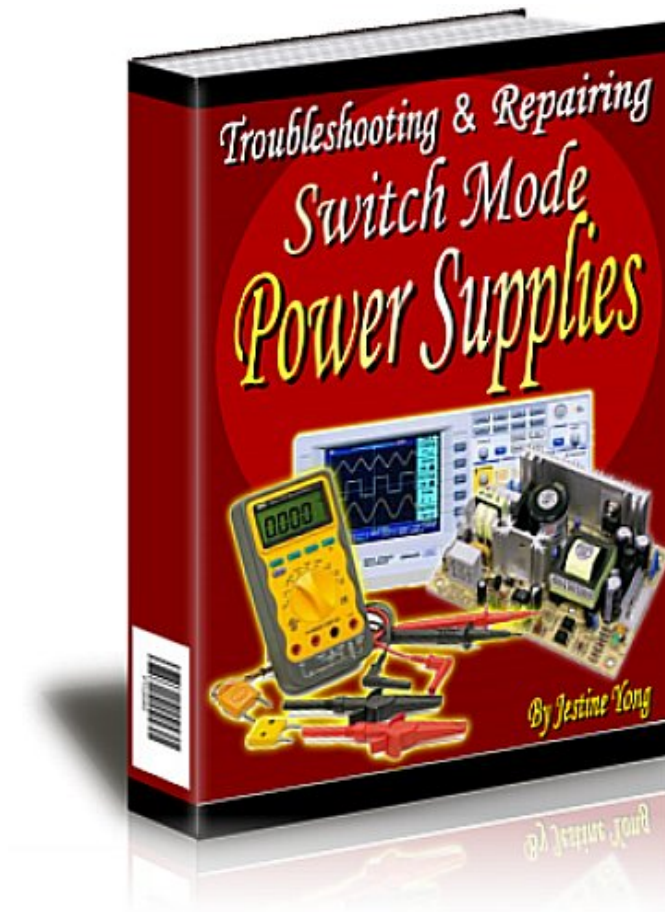


Troubleshooting & Repairing Switch Mode Power Supplies



Brought to you by Jestine Yong

<http://www.PowerSupplyRepairGuide.com>

Content

Part I

Introduction to SMPS

1. Introduction to Switch Mode Power Supplies (SMPS).....	9
2. Identifying Electronic Components in Different Types of SMPS with the Help of Photos.....	14
3. Block Diagram of a Typical SMPS and How It Works.....	18
4. Easy Way To Understand The 11 Circuit Functions of SMPS With The Help Of Schematic Diagrams.....	24
4.1- Input Protection and EMI Filtering Circuit.....	26
4.2- Bridge Circuit.....	27
4.3- Start Up and Run DC Circuit.....	29
4.4- Oscillator Circuit.....	31
4.5- Secondary Output Voltage Circuit.....	34
4.6- Sampling Circuit.....	36
4.7- Error Detection Circuit.....	38
4.8- Feedback Circuit.....	39
4.9- Protection Circuit	40
4.10- Standby Circuit	50
4.11- Power Factor Correction (PFC) Circuit.....	56
5. Electronic Components Found In SMPS and Possible Causes.....	62
6. How To Find The Right Equivalent Components In SMPS Circuit.....	86

Part II

Secrets of SMPS Troubleshooting Techniques

7. Recommended Tools and Test Equipment For Successful SMPS Repair.....	95
7.1-Isolation Transformer.....	96
7.2-Variable Transformer.....	98

7.3-AC Ammeter.....	100
7.4-Analog and Digital Multimeter.....	102
7.5-Digital Capacitance Meter.....	104
7.6-Blue ESR Meter.....	105
7.7-Blue Ring Tester.....	106
7.8-Oscilloscope.....	107
8. Safety Guidelines.....	109
9. Understand The Six Common Problems Found In SMPS....	115
9.1-No Power.....	115
9.2-Low Output Voltage.....	117
9.3-High Output Voltage.....	118
9.4-Power Cycling/Pulsating/Blinking.....	118
9.5-Power Shutdown.....	121
9.6-Intermittent Power Problem.....	121
10. How to Easily Discharge The Main Capacitor In SMPS.....	122
11. How to Easily Perform Voltage Testing On SMPS Circuit...127	
12. How to Use Oscilloscope to Test SMPS Circuit Waveforms.140	
13. Find Out How Useful Is The Series Light Bulb Trick In SMPS Repairs.....	154
13.1-Light Bulb Off.....	156
13.2-Light Bulb Very Bright.....	157
13.2-Light Bulb Pulsating/Blinking (Slow or Fast).....	158
14. The Five Methods That I Use To Troubleshoot And Repair SMPS.....	161
14.1-Using the Blue Ring Tester Method.....	161
14.2-Flickering Method.....	165
14.3-Resistance Test Method.....	168
14.4-Isolation Method.....	170
14.5-Secondary Diode Removal Method.....	177
15. Simple Way For Beginners To Troubleshoot And Repair Any Type Of SMPS By Following My Favourite Method.....	179

16. What Should You Do If Too Many Components Burnt In The SMPS?.....189

17. How To Know If The Substitution Part Number Will Last Or Not.....195

Part III

True Case Histories

18. 11 True Case Histories of SMPS Repair That You Should Not Miss.....200

PART IV

Troubleshooting and Repairing ATX Power Supply

19. Troubleshooting And Repairing ATX Power Supply227

20. ATX Power Supply Repair True Case Histories.....245

Part V

Miscellaneous

21. Understanding Power Supply Glossary Terms.....262

22. Recommended Electronic Repair E-Books.....267

23. Recommended Resources.....269

24. Conclusion.....271

Preview Page

Page 14

2) Identifying Electronic Components In Different Types Of SMPS With The Help Of Photos

I will expose to you different types of SMPS with the help of photos so that you can be familiar with the section and components used in SMPS. With the information provided in the photos, I'm sure you will be well prepared in troubleshooting and repairing SMPS in the future.

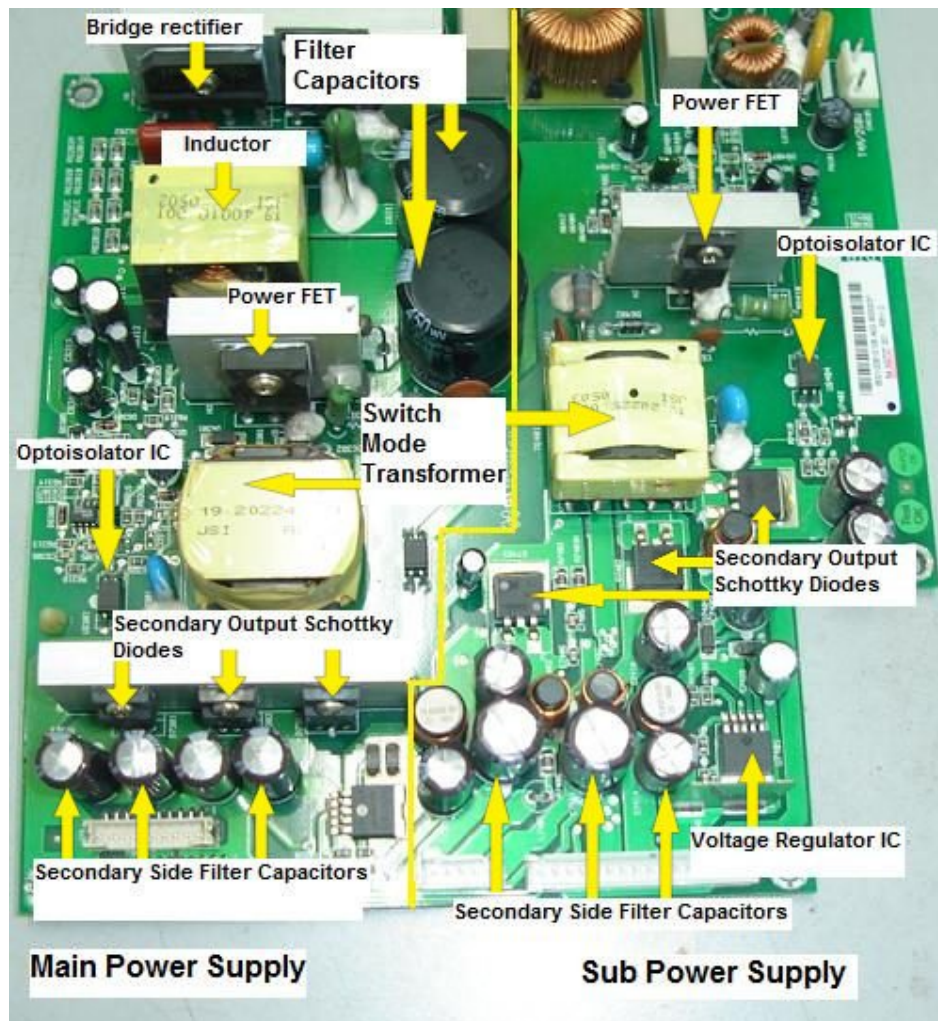


Figure 2.1- A Typical LCD TV SMPS

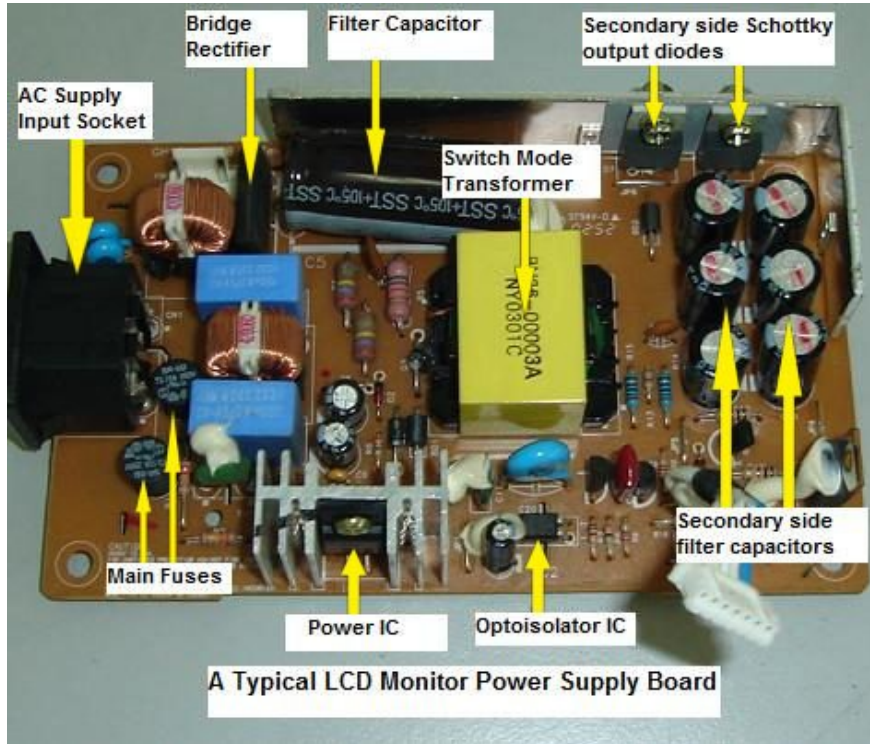


Figure 2.2- A 15" Samsung LCD Monitor SMPS

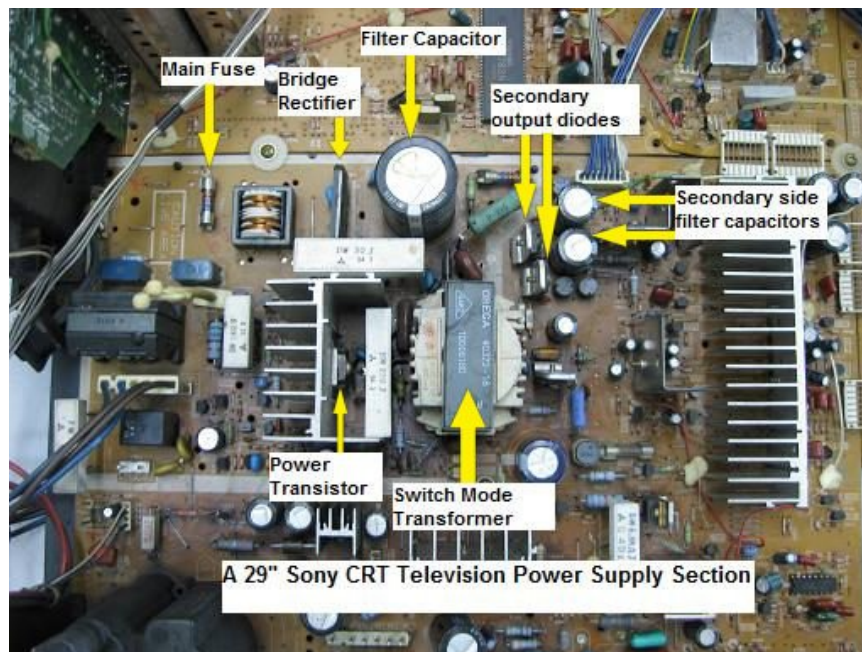


Figure 2.3- A 29" Sony CRT Television SMPS (Primary Side)

If you have seen all the photos, you will notice that almost all of the power supplies

4.2) The Bridge Circuit

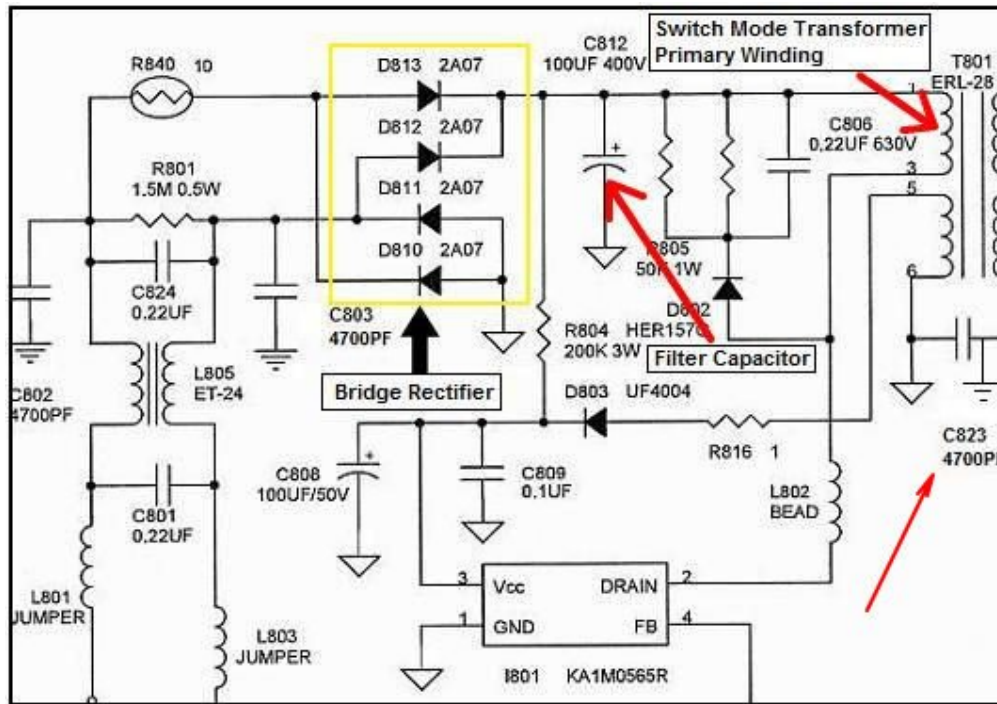


Figure 4.3- The Bridge circuit

The bridge circuit consists of a bridge rectifier (either 4 individual diodes or a single package rectifier) and a filter capacitor. The function of the bridge rectifier is to convert the incoming AC voltage into DC voltage and the filter capacitor (usually have the value of 220uf 400Volt) to remove the ripples and this will provide a nice DC voltage source to the primary winding of switch mode power transformer. For countries that use the 220 to 240 VAC, the DC voltage that you will get is about 300VDC and for countries that use 110-120VAC, the DC voltage that you will get is about 150 to 160 VDC. The DC voltage that you get is measured across the two pins of the filter capacitor using a multimeter. You may refer to chapter 11 on “**How to easily perform voltage testing on SMPS circuit**”.

In some power supply design, you could see that there are capacitors connected across each diode in the bridge rectifier as seen from figure 4.4. The function of the capacitors is to suppress the RFI signals generated by the rectifier diodes.

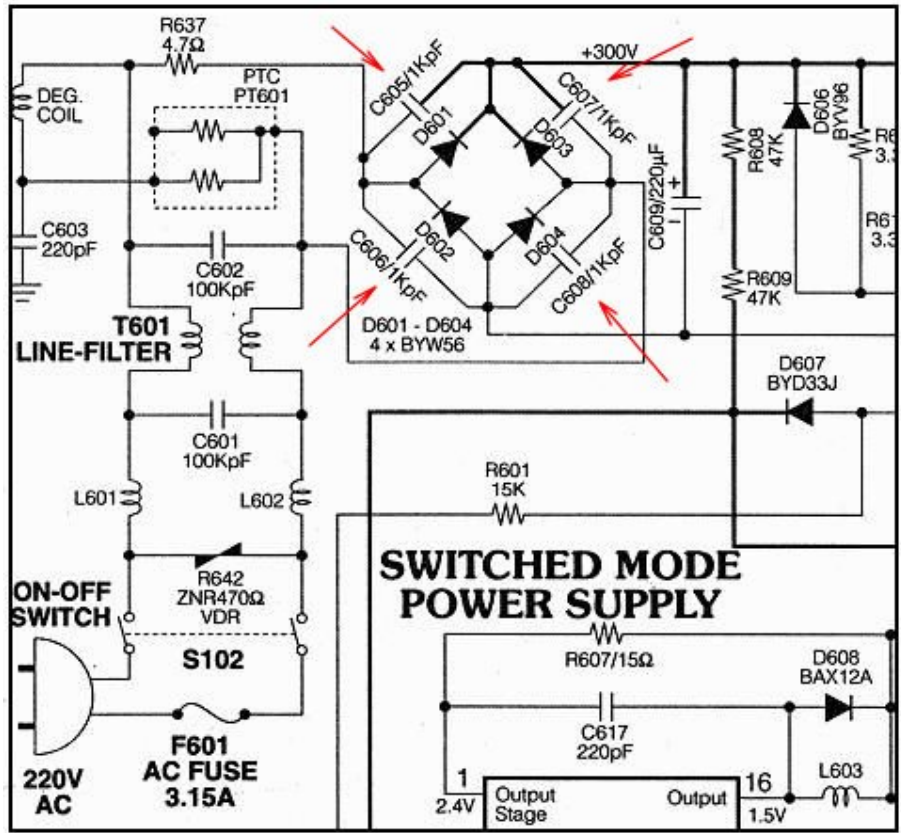


Figure 4.4- Capacitors Connected Across Each Diode In The Bridge Rectifier

If the bridge rectifier is shorted, then the

2 Flickering Method

This method is used to find out whether the primary or the secondary section is the cause of the problem. Sometimes in SMPS repair, you just don't know where the problem lies. You might have checked many of the major components like power FET, secondary output diodes, Horizontal output transistor (HOT), FLYBACK, Yoke coils, B+ coils and etc and all seemed to be good. You need an absolute way to find out which section is actually given you the problem. Once you know which section is having problem then it will be easy for you to spend all your time on that section so that **you can easily nailed down the culprit.**

The first thing that you need to do is to follow the steps below:

- 1 Remove the SMPS transformer from the circuit (refer to figure 14.4)
- 2 Set the analogue multimeter to 50 VDC
- 3 Place the.....

To read the rest of the chapter of “Troubleshooting And Repairing Switch Mode Power Supplies” (271 pages), please visit:

[Http://www.PowerSupplyRepairGuide.com](http://www.PowerSupplyRepairGuide.com)

Don't waste anymore of your precious time to search from the Internet to learn the **basic repair**. In this E-book, you will learn all my **Advance Troubleshooting and Repairing Secrets** and **YOU** can become a **Professional** in Switch Mode Power Supplies repair!

All the best!

Jestine Yong